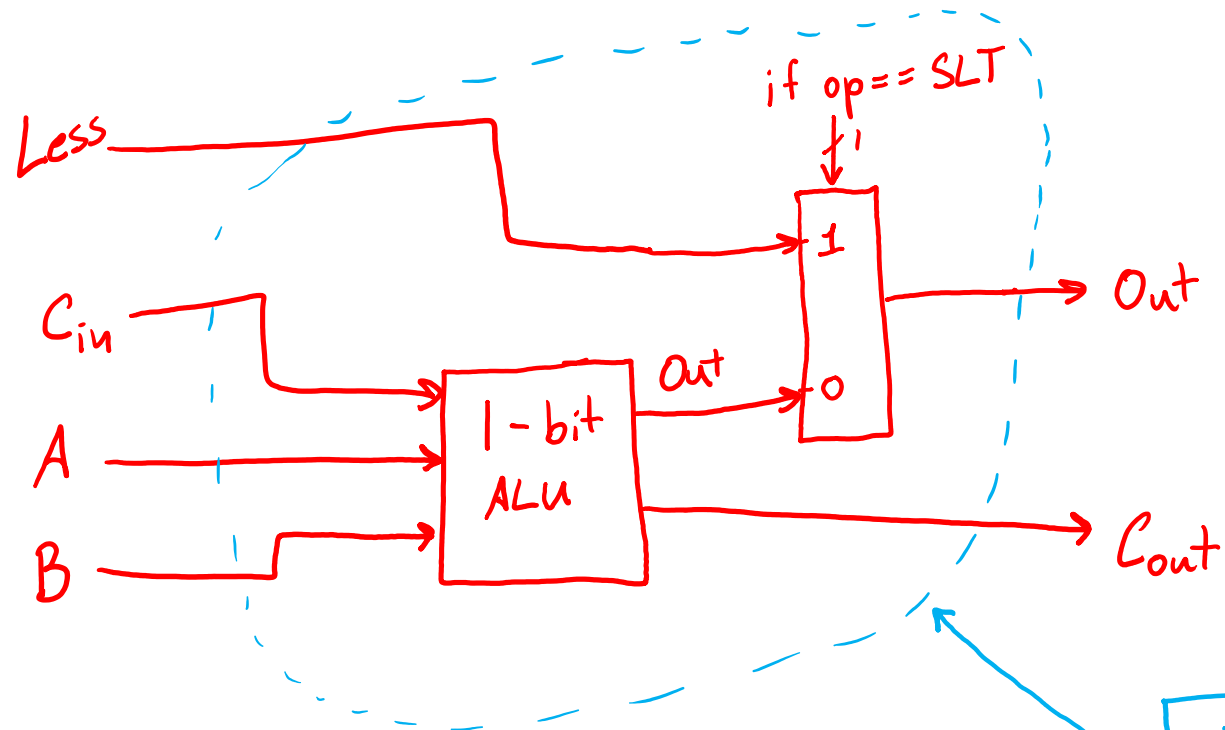


Hardware for Set Less Than


SLT $\rightarrow$ if ($A < B$) then Out = 1, else Out = 0




- Homework #1 due next Monday
- Lab 2 progress check today
- no class this Friday or next Monday

1-bit
ALU w/
SLT

Hardware for Set Less Than

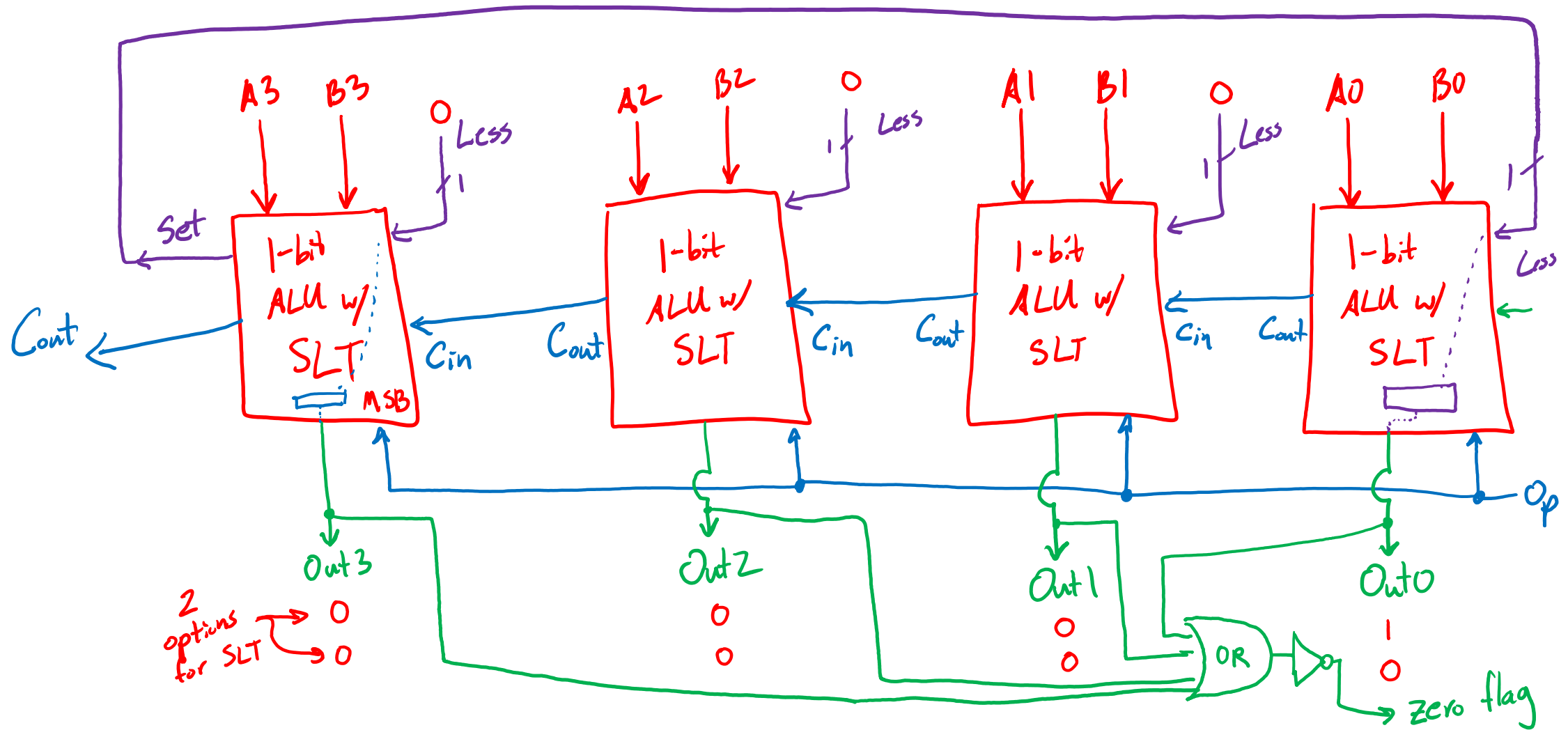

Hardware for Most Significant Bit

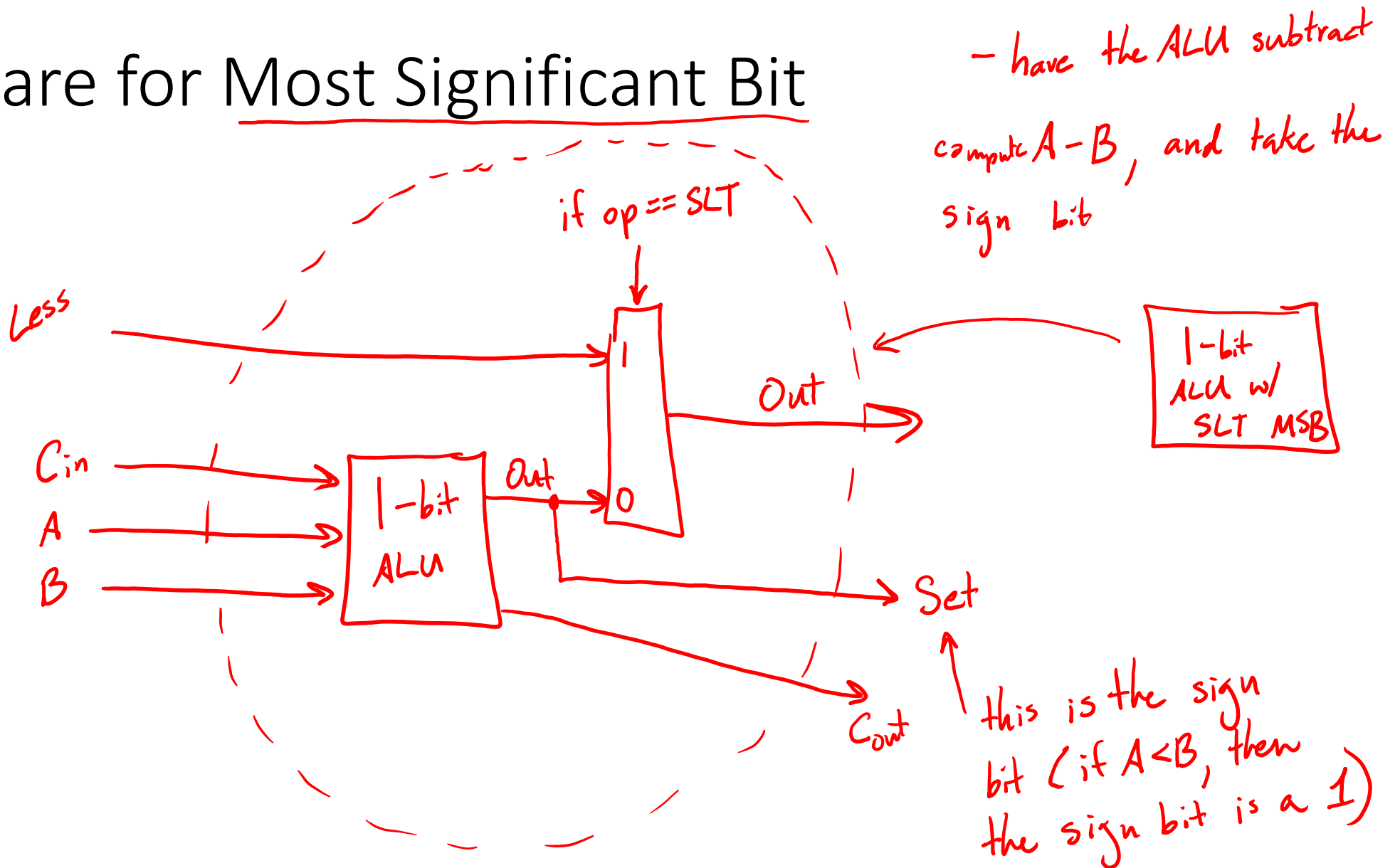


Hardware for Set Less Than

- have the ALUs do a subtract internally
- run the sign bit into the Less input of LSB ALU

Hardware for BNE and BEQ

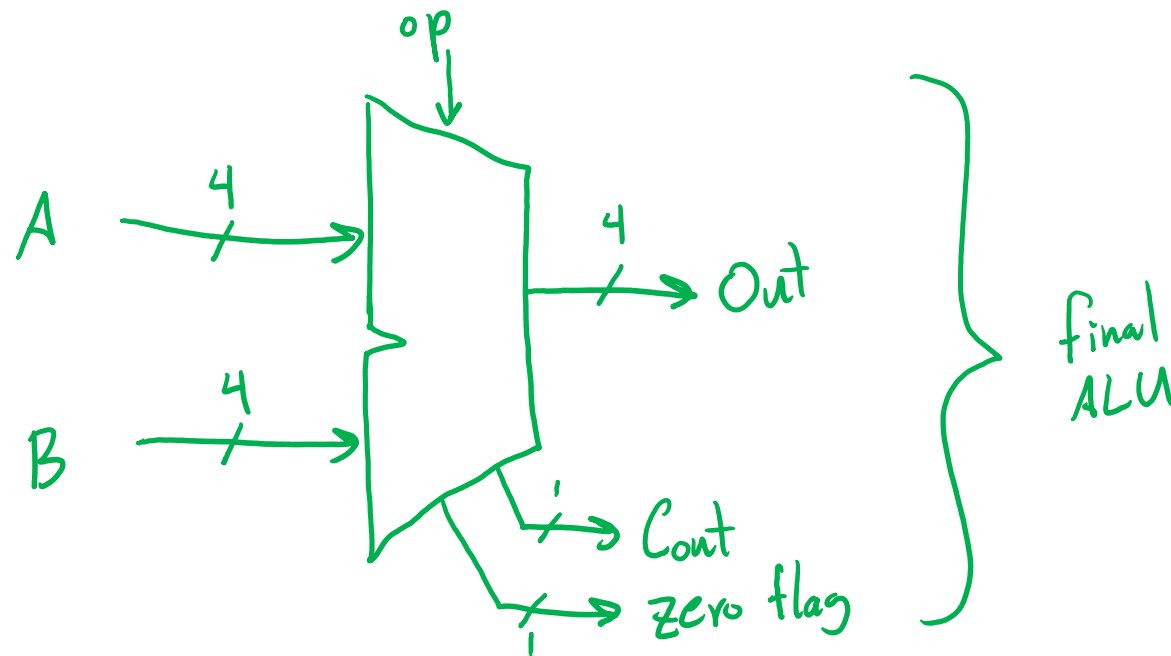- zero flag is set high only when the ALU output is the number 0



Datapath and Control

4.1-4.4

Goal

- Build an architecture to support the following instructions:

arithmetic: [✓]add, [✓]sub, [✓]addi, [✓]slt

memory : [✓]lw, [✓]sw

branches: [✓]beq, [✓]j

MIPS Instruction Trends

- Read 2 regs: add, sub, slt, beq, sw
- 3 regs: X
- 1 reg: addi, lw
- 0 reg: j
- Write: add, sub, addi, lw, slt

Framework


- Makefile

- make lab2


- hand in all java source
and the Makefile

- Lab 2

- name top level
class 'lab2'

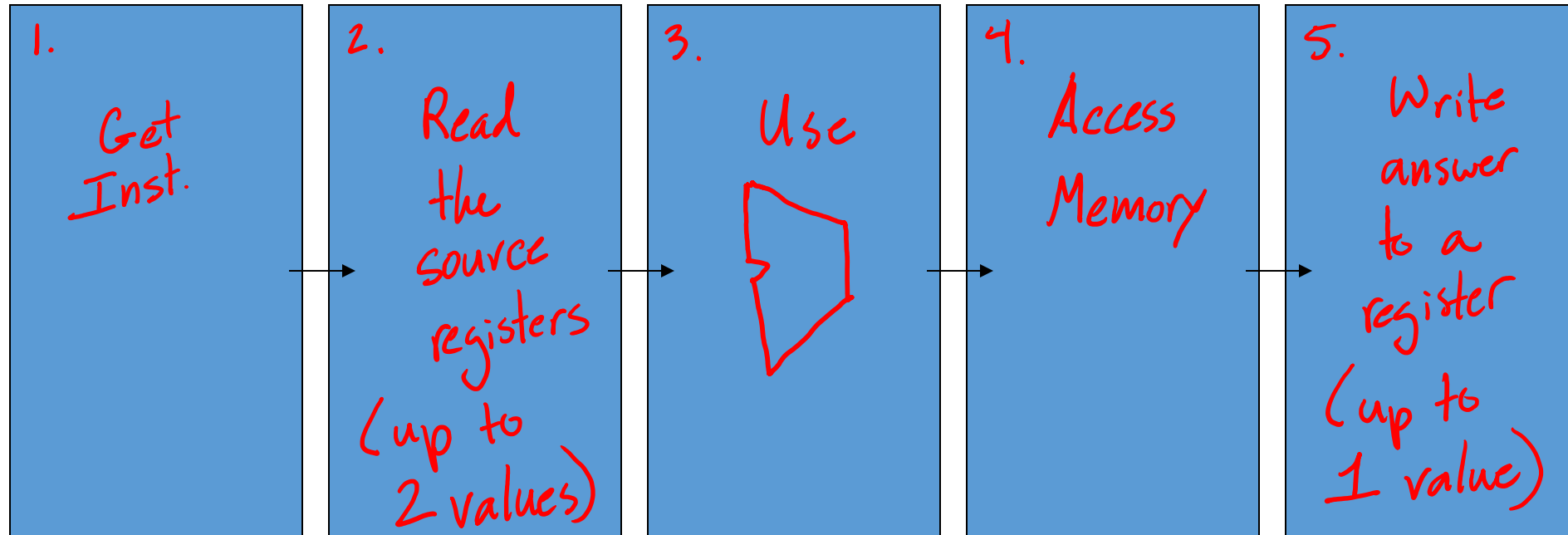

1. Get Instruction

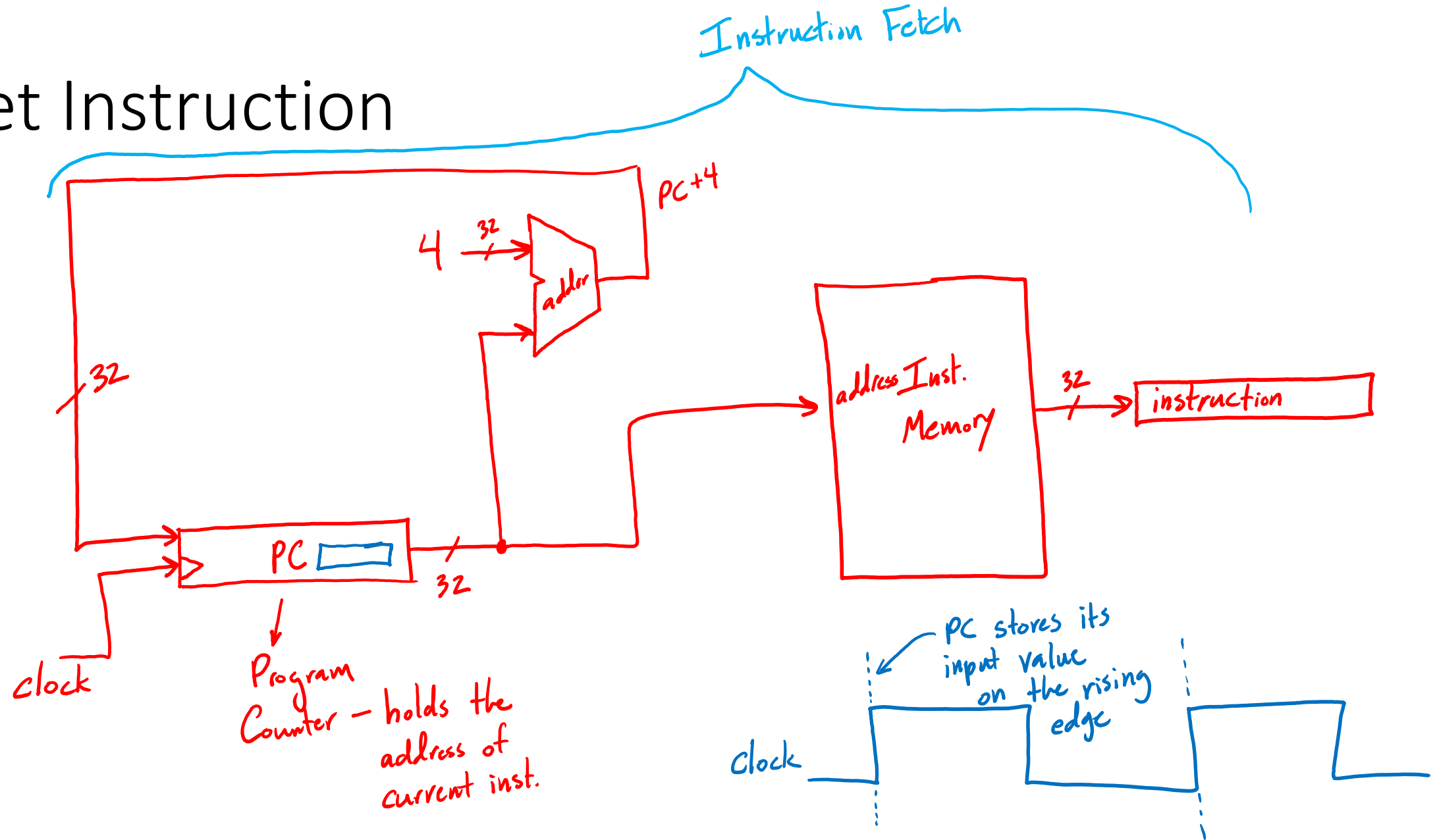

Instruction Fetch

- Key Points:

- PC is a register (clocked unit)
- updates on the rising edge
- inst. memory is not clocked unit

2. Register File - structure that holds all the register data

- 32 regs. x 32 bits

- Read 2 registers

- Write 1 register

Register File

