

ALU Construction

ALU (Arithmetic Logic Unit)

- arithmetic ops.

- logical ops.

- branch computation

- address computation

Decide which operations to support


Operation	OpCode
1. And	00
2. Or	01
3. Add	10
4. Sub	11

- Choose operations
- Assign op-codes


Design 1-bit for each operation

And & Or

1.

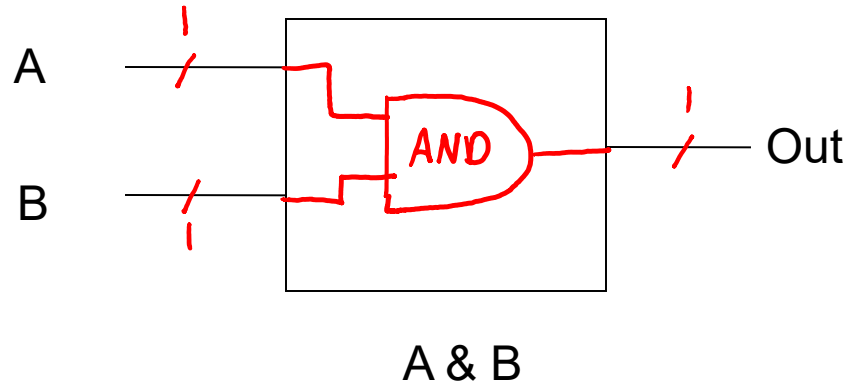

2.

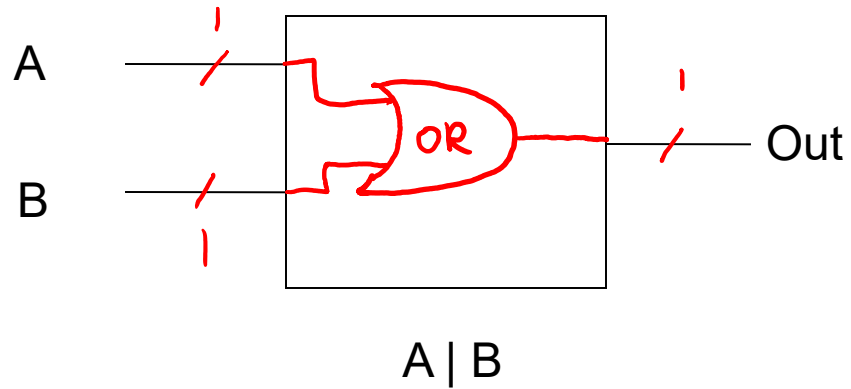



Design 1-bit for each operation

inputs		outputs		
A	B	Cin	Cout	Out
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

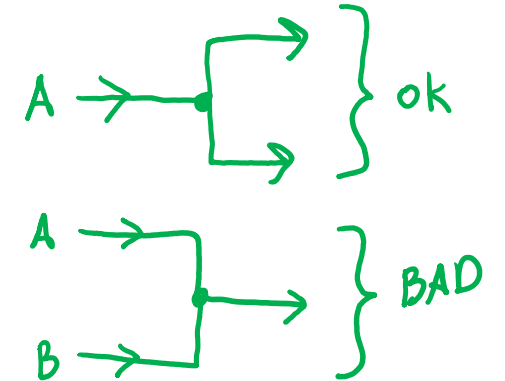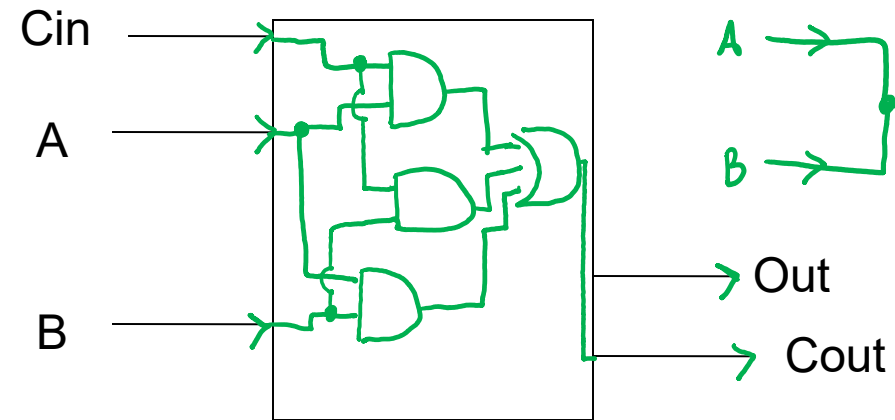3. Add


$$C_{out} = \overset{\text{and}}{A \cdot B} + \overset{\text{or}}{A \cdot C_{in}} + B \cdot C_{in}$$

$$Out = A \text{ XOR } B \text{ XOR } C_{in}$$




$$\begin{array}{r}
 \text{Cout} \\
 11 \\
 0110 \quad A \\
 + 0011 \quad B \\
 \hline
 1001 \quad \text{Out}
 \end{array}$$

A + B

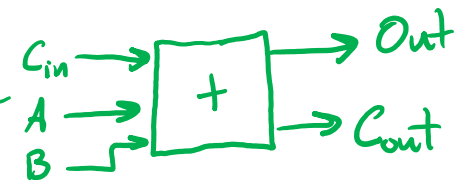

Design 1-bit for each operation

4. Sub

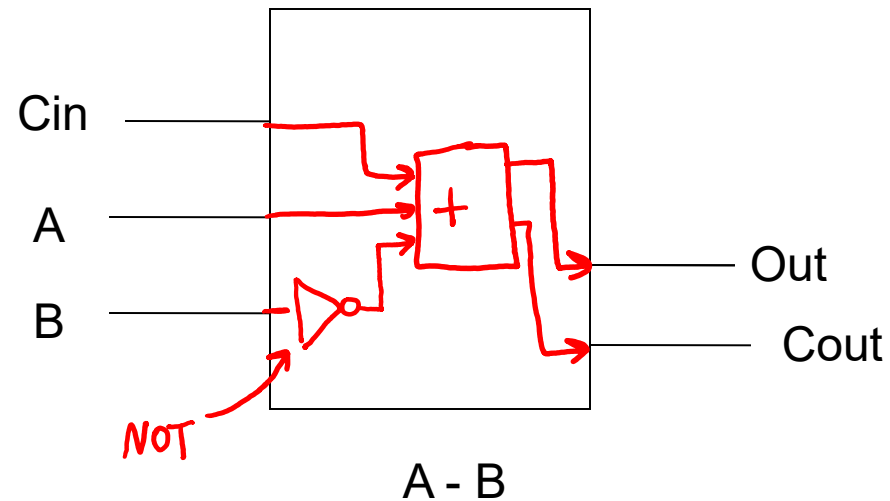


$$A - B = A + (-B)$$

- to compute subtract,
flip B, but
we need to add
1 later

0110
- 0011 →

Use MUX to choose between results

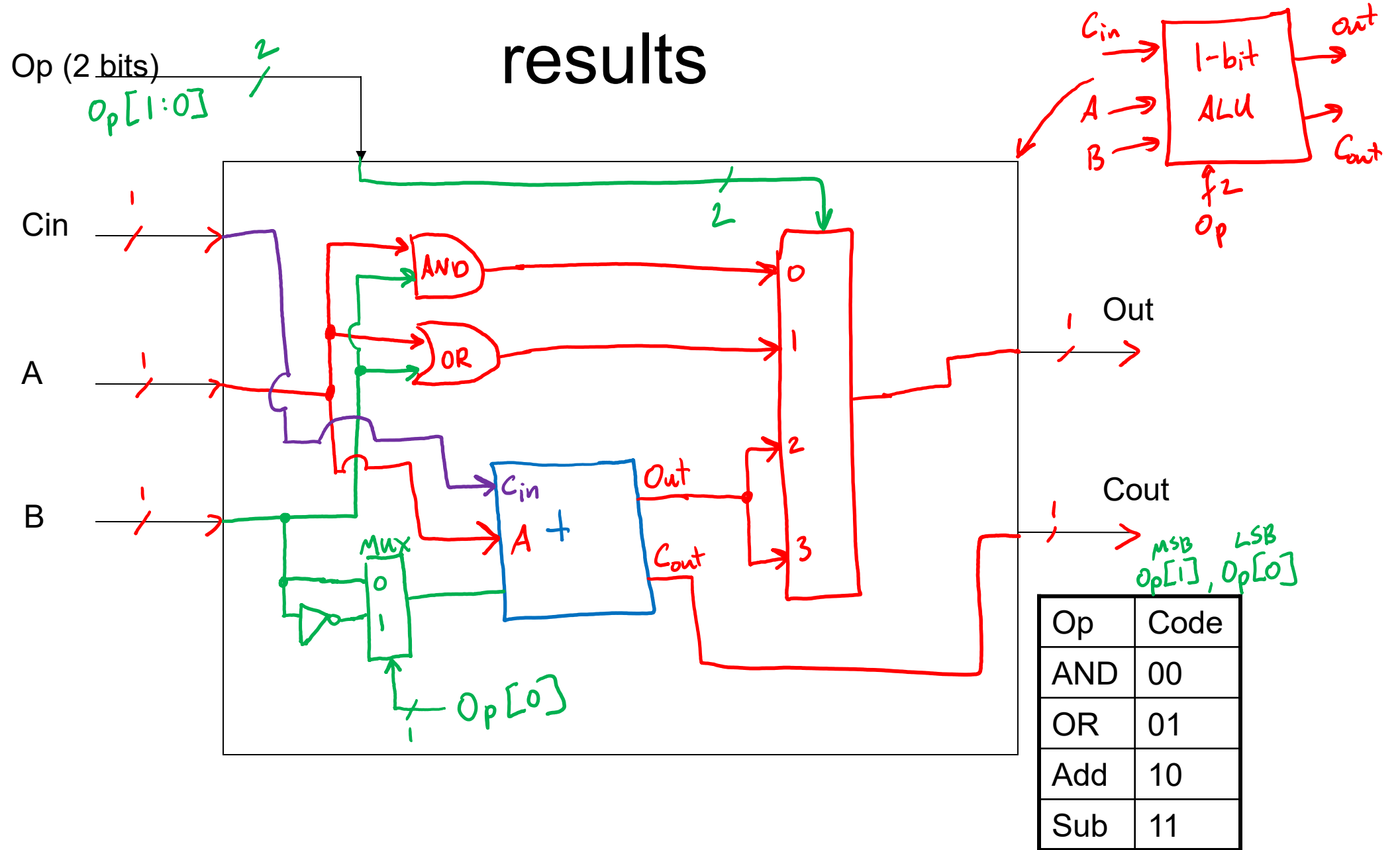

4-bit ALU

